

Team Members:

1. Aditya Prakash Borate (23110065)
2. Haarit Ravindrakumar Chavda (23110077)

Complete Tiny Processor

- Synthesizable Design Code

- ProgramMemory.v

```
1. Arithmetic Demo: ADD, SUB, INC, DEC, MOV, NOP, HLT
`timescale 1ns / 1ps
module ProgramMemory(
    input  [3:0] PC,
    output reg [7:0] Instruction
);
    reg [7:0] MEMORY [15:0];
    initial begin
        MEMORY[0] = 8'b0000_0000; // NOP
        MEMORY[1] = 8'b1001_0001; // MOV ACC,R1
        MEMORY[2] = 8'b0001_0010; // ADD R2
        MEMORY[3] = 8'b0010_0011; // SUB R3
        MEMORY[4] = 8'b0000_0110; // INC ACC
        MEMORY[5] = 8'b0000_0111; // DEC ACC
        MEMORY[6] = 8'b1010_0100; // MOV R4,ACC
        MEMORY[7] = 8'b1111_1111; // HLT
        MEMORY[8] = 8'b0000_0000;
        MEMORY[9] = 8'b0000_0000;
        MEMORY[10] = 8'b0000_0000;
        MEMORY[11] = 8'b0000_0000;
        MEMORY[12] = 8'b0000_0000;
        MEMORY[13] = 8'b0000_0000;
        MEMORY[14] = 8'b0000_0000;
        MEMORY[15] = 8'b1111_1111;
    end
    always @(*) Instruction = MEMORY[PC];
endmodule

// 2. MUL & SUB Demo: MUL, SUB, HLT
//`timescale 1ns / 1ps
//module ProgramMemory(
//    // input  [3:0] PC,
//    // output reg [7:0] Instruction
//);
//    // reg [7:0] MEMORY [15:0];
//    // initial begin
```

```
// MEMORY[0] = 8'b1001_0001; // MOV ACC,R1
// MEMORY[1] = 8'b0011_0010; // MUL R2
// MEMORY[2] = 8'b0010_0011; // SUB R3
// MEMORY[3] = 8'b1111_1111; // HLT
// MEMORY[4] = 8'b0000_0000;
// MEMORY[5] = 8'b0000_0000;
// MEMORY[6] = 8'b0000_0000;
// MEMORY[7] = 8'b0000_0000;
// MEMORY[8] = 8'b0000_0000;
// MEMORY[9] = 8'b0000_0000;
// MEMORY[10] = 8'b0000_0000;
// MEMORY[11] = 8'b0000_0000;
// MEMORY[12] = 8'b0000_0000;
// MEMORY[13] = 8'b0000_0000;
// MEMORY[14] = 8'b0000_0000;
// MEMORY[15] = 8'b1111_1111;
// end
// always @(*) Instruction = MEMORY[PC];
//endmodule
```

```
// 3. All shifts + AND, XRA, NOP, HLT
//timescale 1ns / 1ps
//module ProgramMemory(
//  input [3:0] PC,
//  output reg [7:0] Instruction
//);
// reg [7:0] MEMORY [15:0];
// initial begin
//   MEMORY[0] = 8'b0000_0000; // NOP
//   MEMORY[1] = 8'b1001_0001; // MOV ACC,R1
//   MEMORY[2] = 8'b0000_0001; // LSL ACC
//   MEMORY[3] = 8'b0000_0010; // LSR ACC
//   MEMORY[4] = 8'b0000_0011; // CIR ACC
//   MEMORY[5] = 8'b0000_0100; // CIL ACC
//   MEMORY[6] = 8'b0000_0101; // ASR ACC
//   MEMORY[7] = 8'b0101_0010; // AND R2
//   MEMORY[8] = 8'b0110_0011; // XRA R3
//   MEMORY[9] = 8'b1111_1111; // HLT
//   // fill with NOP
//   MEMORY[10] = 8'b0000_0000;
//   MEMORY[11] = 8'b0000_0000;
//   MEMORY[12] = 8'b0000_0000;
//   MEMORY[13] = 8'b0000_0000;
//   MEMORY[14] = 8'b0000_0000;
//   MEMORY[15] = 8'b1111_1111;
// end
// always @(*) Instruction = MEMORY[PC];
//endmodule
```

```
// 4. Branch & Return Demo: CMP, Br, Ret, MOV, HLT
//timescale 1ns / 1ps
//module ProgramMemory(
```

```

// input [3:0] PC,
// output reg [7:0] Instruction
//);
// reg [7:0] MEMORY [15:0];
// initial begin
//     // If R1 < R2 then load ACC?R4 else ACC?R3; then save to R5, return to HLT
//     MEMORY[0] = 8'b1001_0001; // MOV ACC,R1
//     MEMORY[1] = 8'b0111_0010; // CMP R2
//     MEMORY[2] = 8'b1000_0101; // Br 5
//     MEMORY[3] = 8'b1001_0011; // MOV ACC,R3
//     MEMORY[4] = 8'b1000_0110; // Br 6
//     MEMORY[5] = 8'b1001_0100; // MOV ACC,R4
//     MEMORY[6] = 8'b1010_0101; // MOV R5,ACC
//     MEMORY[7] = 8'b1011_1001; // RET 9
//     MEMORY[8] = 8'b0000_0000; // NOP (dead)
//     MEMORY[9] = 8'b1111_1111; // HLT
//     // unused
//     MEMORY[10] = 8'b0000_0000;
//     MEMORY[11] = 8'b0000_0000;
//     MEMORY[12] = 8'b0000_0000;
//     MEMORY[13] = 8'b0000_0000;
//     MEMORY[14] = 8'b0000_0000;
//     MEMORY[15] = 8'b1111_1111;
// end
// always @(*) Instruction = MEMORY[PC];
//endmodule

```

//5. Upto counter upto 15

//timescale 1ns / 1ps

```

//module ProgramMemory(
// input [3:0] PC,
// output reg [7:0] Instruction
//);
// reg [7:0] MEMORY [15:0];
// initial begin
//     //Increment ACC (starting from R1) until it equals R15

//     MEMORY[0] = 8'b1001_0000; // MOV ACC, R1
//     MEMORY[1] = 8'b0000_0110; // INC ACC
//     MEMORY[2] = 8'b0111_1111; // CMP R15
//     MEMORY[3] = 8'b1000_0001; // Br 2
//     MEMORY[4] = 8'b1111_1111; // HLT
//     MEMORY[5] = 8'b1111_1111; // HLT

//     MEMORY[6] = 8'b0000_0000;
//     MEMORY[7] = 8'b0000_0000;
//     MEMORY[8] = 8'b0000_0000;
//     MEMORY[9] = 8'b0000_0000;
//     MEMORY[10] = 8'b0000_0000;
//     MEMORY[11] = 8'b0000_0000;
//     MEMORY[12] = 8'b0000_0000;
//     MEMORY[13] = 8'b0000_0000;
//     MEMORY[14] = 8'b0000_0000;

```

```
//    MEMORY[15] = 8'b1111_1111;
//  end

//  always @(*) begin
//    Instruction = MEMORY[PC];
//  end
//endmodule
```

- Registerfile.v

```
`timescale 1ns / 1ps
module Register #(
  parameter INIT_VAL = 8'd0
)(
  input clk,
  input we,
  input [7:0] d,
  output reg [7:0] q
);
  initial begin
    q = INIT_VAL;
  end

  always @(posedge clk) begin
    if (we)
      q <= d;
    end
endmodule

module RegisterFile (
  input clk,
  input [3:0] Addr,      // Address to read/write
  input [7:0] WriteData, // Data to write
  input WriteEnable,     // Write enable signal
  output [7:0] ReadData  // Output data
);
  wire [7:0] reg_out [15:0];
  reg [15:0] we_vector;

  integer i;
  always @(*) begin
    for (i = 0; i < 16; i = i + 1)
      we_vector[i] = (WriteEnable && (Addr == i));
    end

  // Generate 16 Register Instances
  genvar idx;
  generate
    for (idx = 0; idx < 16; idx = idx + 1) begin : reg_block
      Register #(INIT_VAL(idx)) reg_inst (
        .clk(clk),
        .we(we_vector[idx]),
        .d(WriteData),
        .q(reg_out[idx])
      )
    end
  endgenerate
endmodule
```

```

    );
    end
endgenerate

    assign ReadData = reg_out[Addr];

endmodule

```

- ALU.v

```

`timescale 1ns / 1ps
// ALU: Performs Arithmetic and Logical Operations
module ALU (
    input [7:0] ACC,      // Accumulator input
    input [7:0] Ri,       // Register input
    input [7:0] Opcode,   // Instruction Opcode
    output reg [7:0] Result, // ALU output
    output reg CB,        // Carry/Borrow
    output reg [7:0] EXT   // Extended register for MUL result
);
    reg [8:0] temp;
    reg [15:0] temp_mul;

    initial begin
        // Default output assignments
        Result = ACC;
        CB = 0;
        EXT = 0;
    end

    always @(*) begin

        case (Opcode[7:4])
            4'b0001: begin // ADD
                temp = {1'b0, ACC} + {1'b0, Ri};
                Result = temp[7:0];
                CB = temp[8];
            end
            4'b0010: begin // SUB
                temp = {1'b0, ACC} - {1'b0, Ri};
                Result = temp[7:0];
                CB = temp[8];
            end
            4'b0011: begin // MUL
                temp_mul = ACC * Ri;
                Result = temp_mul[7:0];
                EXT = temp_mul[15:8];
            end
            4'b0101: begin // AND
                Result = ACC & Ri;
            end
            4'b0110: begin // XRA Ri (bitwise XOR)

```

```

        Result = ACC ^ Ri;
    end
    4'b0111: begin // CMP Ri (Compare ACC with Ri)
        // If ACC > Ri then CB is set to 1, otherwise 0.
        CB = (ACC < Ri) ? 1'b1 : 1'b0;
    end
    4'b0000: begin // Shift, Increment, Decrement operations
        case (Opcode[3:0])
            4'b0001: Result = ACC << 1;           // Logical Shift Left
            4'b0010: Result = ACC >> 1;           // Logical Shift Right
            4'b0011: Result = {ACC[0], ACC[7:1]}; // Circuit (rotate) right
            4'b0100: Result = {ACC[6:0], ACC[7]}; // Circuit (rotate) left
            4'b0101: Result = {ACC[7], ACC[7:1]}; // Arithmetic Shift Right
            4'b0110: begin                          // Increment ACC
                temp = {1'b0, ACC} + 9'd1;
                Result = temp[7:0];
                CB = temp[8];
            end
            4'b0111: begin                          // Decrement ACC
                temp = {1'b0, ACC} - 9'd1;
                Result = temp[7:0];
                CB = temp[8];
            end
            default: Result = ACC; // default case for undefined sub-opcodes
        endcase
    end
    default: Result = ACC; // default case for undefined opcodes
endcase
end
endmodule

```

- Processor.v

```

`timescale 1ns / 1ps

// Top module for processor
module Processor (
    input clk,
    input rstn,
    output reg [7:0] ACC
);
    // Program counter
    reg [3:0] PC;

    // Extra space to store result of multiplication
    wire [7:0] EXT;

    // Carry bit for addition , subtractor and for branch instruction
    wire CB;

    // Wires for connecting instructions from program memory to input of alu
    wire [7:0] Instruction;

    // Wires to connect the active register to input of alu
    wire [7:0] RegData;

```

```
// Wires to connect the result of alu to accumulator
wire [7:0] ALUResult;

// Storage to extract address from operation code
reg [3:0] Addr;

// Flags for write,branch,return and halt
reg WriteEnable;
reg IsBranch;
reg IsRet;
reg IsHalt;

// Instantiating all the modules
ProgramMemory U1(PC, Instruction);
RegisterFile U2(clk, Addr, ACC, WriteEnable, RegData );
ALU U3(ACC, RegData, Instruction, ALUResult, CB, EXT);

// Decoding the operation code
always @(*) begin
    Addr = Instruction[3:0];
    WriteEnable = 0;
    IsBranch = 0;
    IsRet = 0;
    IsHalt = 0;

    case (Instruction[7:4])
        4'b1010: WriteEnable = 1;
        4'b1000: IsBranch = 1;
        4'b1011: IsRet = 1;
        4'b1111: IsHalt = 1;
    endcase
end

always @(posedge clk or negedge rstn) begin

    // reset
    if (!rstn) begin
        PC <= 4'd0;
        ACC <= 8'd0;
    end

    else begin
        // Either move data from register or update the acc by alu result
        case (Instruction[7:4])
            4'b1001: ACC <= RegData;

            default: ACC <= ALUResult;
        endcase

        // Branching Condition
        if (IsBranch && CB)
```

```
        PC <= Instruction[3:0];
    // Return condition
    else if (IsRet)
        PC <= Instruction[3:0];
    // Halting condition
    else if (!IsHalt)
        PC <= PC + 1;
    else
        PC <= PC;
    end
end
endmodule
```

• Testbench Code

- ProgramMemory_tb.v

```
`timescale 1ns / 1ps

module ProgramMemory_tb;

    reg [3:0] PC;
    wire [7:0] Instruction;

    // Instantiate the ProgramMemory module
    ProgramMemory uut (
        .PC(PC),
        .Instruction(Instruction)
    );

    integer i;

    initial begin
        // Loop through all possible PC values (0 to 15)
        for (i = 0; i < 16; i = i + 1) begin
            PC = i[3:0];
            #10; // Wait for 10 ns to allow Instruction to update
        end
        #10; // Final delay before simulation ends
        $finish;
    end
endmodule
```

- Registerfile_tb.v

```
`timescale 1ns / 1ps

module RegisterFile_tb;
    reg clk;
    reg [3:0] Addr;
    reg [7:0] WriteData;
```



```

reg WriteEnable;
wire [7:0] ReadData;

RegisterFile uut (
    .clk(clk),
    .Addr(Addr),
    .WriteData(WriteData),
    .WriteEnable(WriteEnable),
    .ReadData(ReadData)
);

initial begin
    $display("Time\tWriteEnable\tAddr\tWriteData\tReadData");
    $monitor("%g\t%b\t\t%h\t%h\t\t%h", $time, WriteEnable, Addr, WriteData,
ReadData);
end

initial begin
    clk = 0;
    forever #5 clk = ~clk; // 10ns clock period
end

initial begin
    // Read default value
    WriteEnable = 0;
    Addr = 4'd2; #10;

    // Write 0xAA to register 2
    WriteEnable = 1;
    Addr = 4'd2;
    WriteData = 8'hAA; #10;

    // Read back from register 2
    WriteEnable = 0;
    Addr = 4'd2; #10;

    // Write 0xFF to register 5
    WriteEnable = 1;
    Addr = 4'd5;
    WriteData = 8'hFF; #10;

    // Read back from register 5
    WriteEnable = 0;
    Addr = 4'd5; #10;

    $finish;
end
endmodule

```

- ALU_tb.v

```

`timescale 1ns / 1ps

module ALU_tb;
    reg [7:0] ACC;

```

```

reg [7:0] Ri;
reg [7:0] Opcode;
wire [7:0] Result;
wire CB;
wire [7:0] EXT;

ALU uut (
    .ACC(ACC),
    .Ri(Ri),
    .Opcode(Opcode),
    .Result(Result),
    .CB(CB),
    .EXT(EXT)
);

initial begin
    // ADD R1
    ACC = 8'd10; Ri = 8'd20; Opcode = 8'b0001_0001; #10;

    // SUB R2
    ACC = 8'd30; Ri = 8'd25; Opcode = 8'b0010_0010; #10;

    // MUL R3
    ACC = 8'd5; Ri = 8'd4; Opcode = 8'b0011_0011; #10;

    // AND R4
    ACC = 8'b10101010; Ri = 8'b11110000; Opcode = 8'b0101_0100; #10;

    // XRA R5
    ACC = 8'b10101010; Ri = 8'b11110000; Opcode = 8'b0110_0101; #10;

    // CMP R6
    ACC = 8'd10; Ri = 8'd15; Opcode = 8'b0111_0110; #10;

    // LSL ACC
    ACC = 8'b00001111; Ri = 8'd0; Opcode = 8'b0000_0001; #10;

    // LSR ACC
    ACC = 8'b11110000; Ri = 8'd0; Opcode = 8'b0000_0010; #10;

    // INC ACC
    ACC = 8'd255; Ri = 8'd0; Opcode = 8'b0000_0110; #10;

    // DEC ACC
    ACC = 8'd0; Ri = 8'd0; Opcode = 8'b0000_0111; #10;

    $finish;
end
endmodule

```

- Processor_tb.v

```

`timescale 1ns / 1ps

module Processor_tb;

```

```
reg clk;
reg rstn;
wire [7:0] ACC;

Processor uut (
    .clk(clk),
    .rstn(rstn),
    .ACC(ACC)
);

initial begin
    $display("Time\tPC\tInstruction\tACC\tOutput");
end

// Clock generation
initial begin
    clk = 0;
    forever #5 clk = ~clk;
end


// Reset and run
initial begin
    rstn = 0; #12;
    rstn = 1;
end

// Stop simulation after instruction 18 (HLT)
initial begin
    #300;
    $finish;
end


endmodule
```

● Simulation Results of Individual Components


1. ProgramMemory_tb

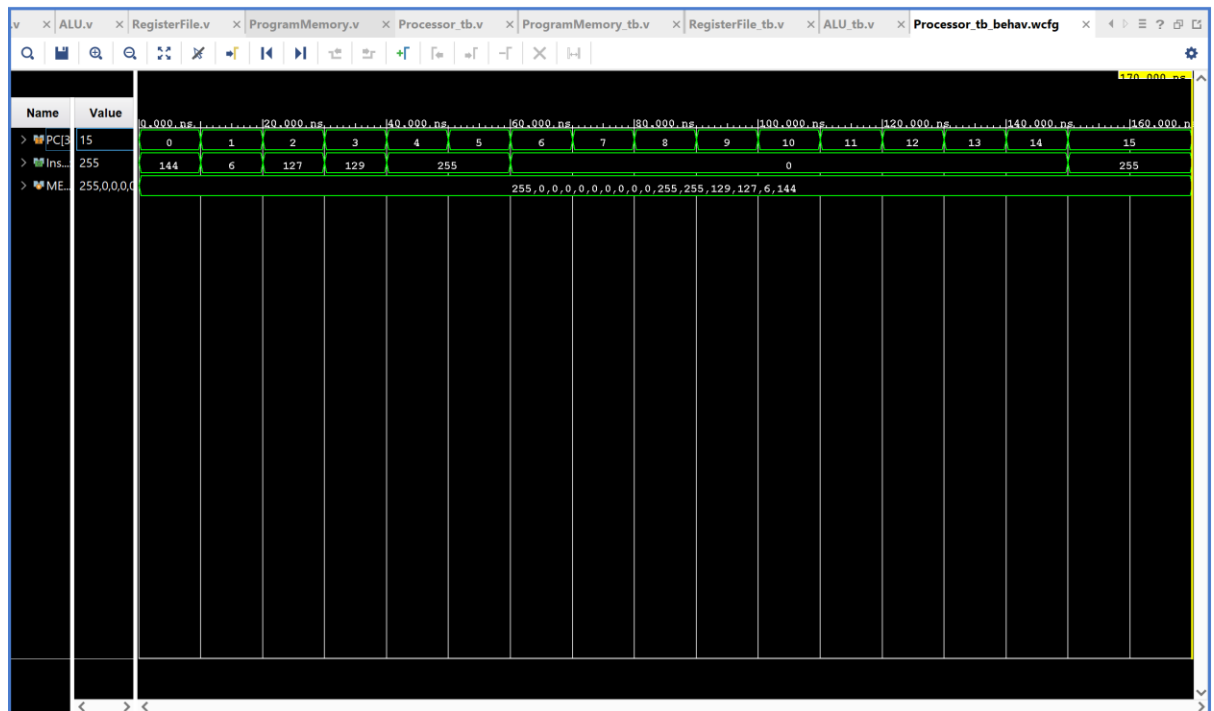

2. RegisterFile_tb

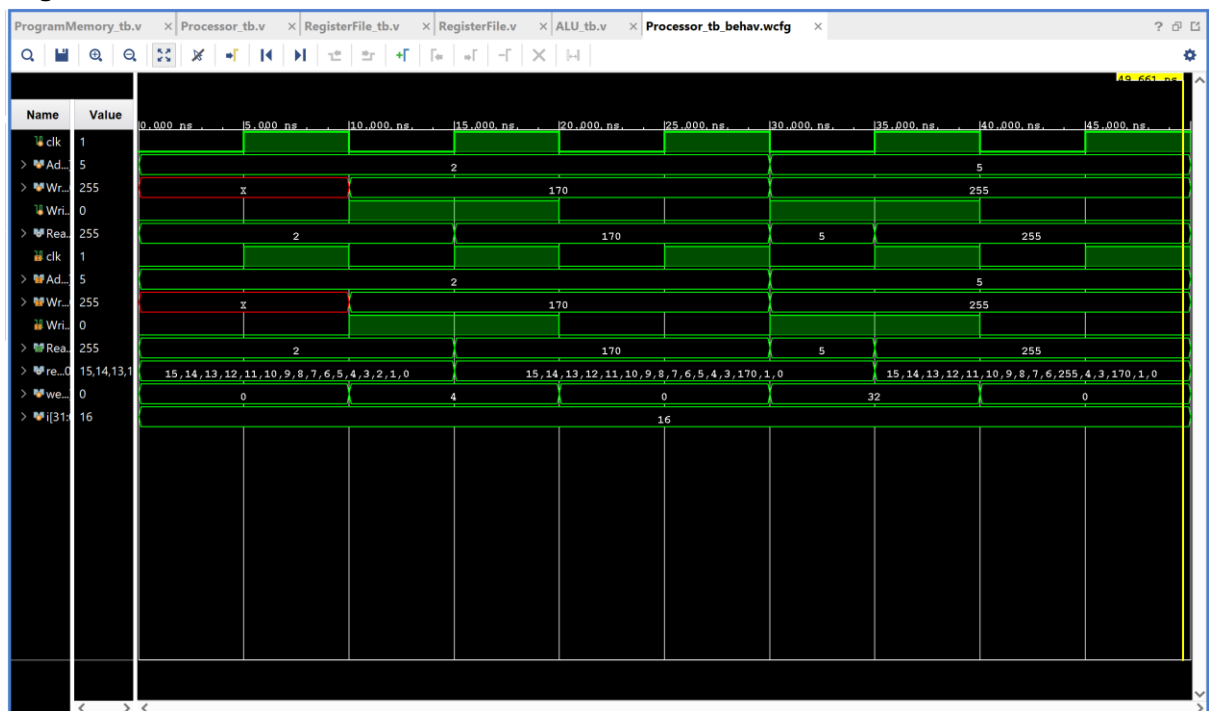


3. ALU_tb

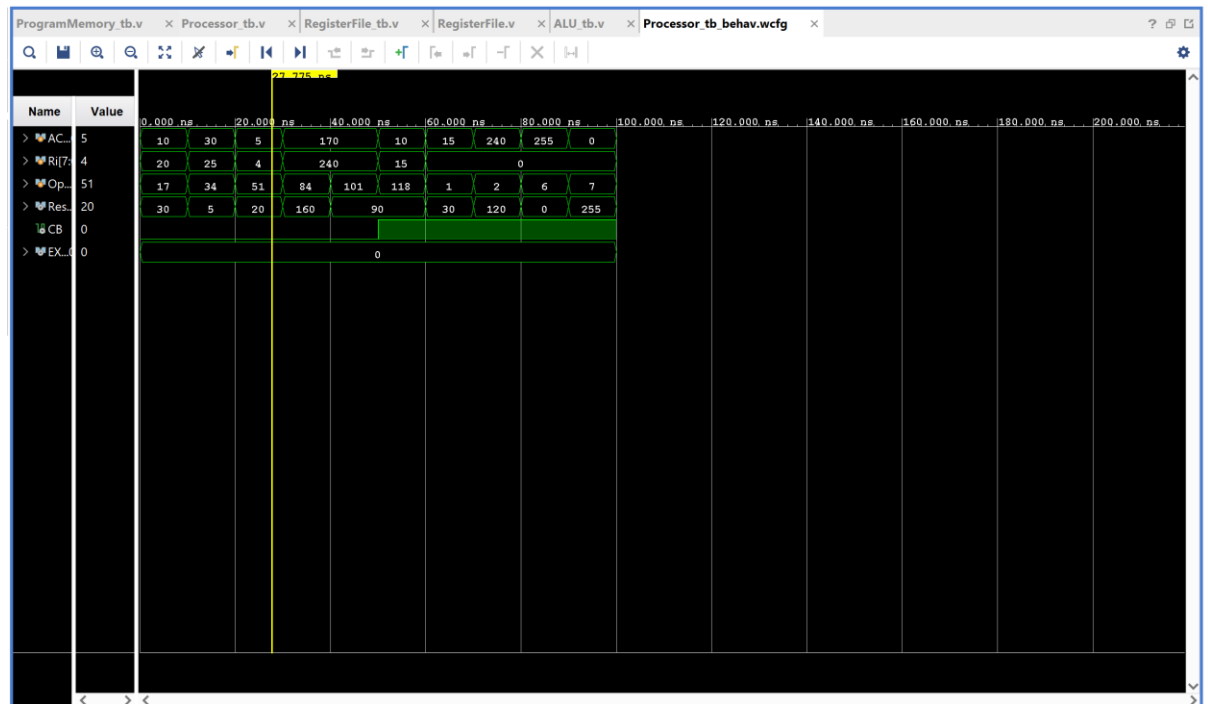


• Simulation Results of Processor


1. ADD, SUB, INC, DEC, MOV, NOP, HLT

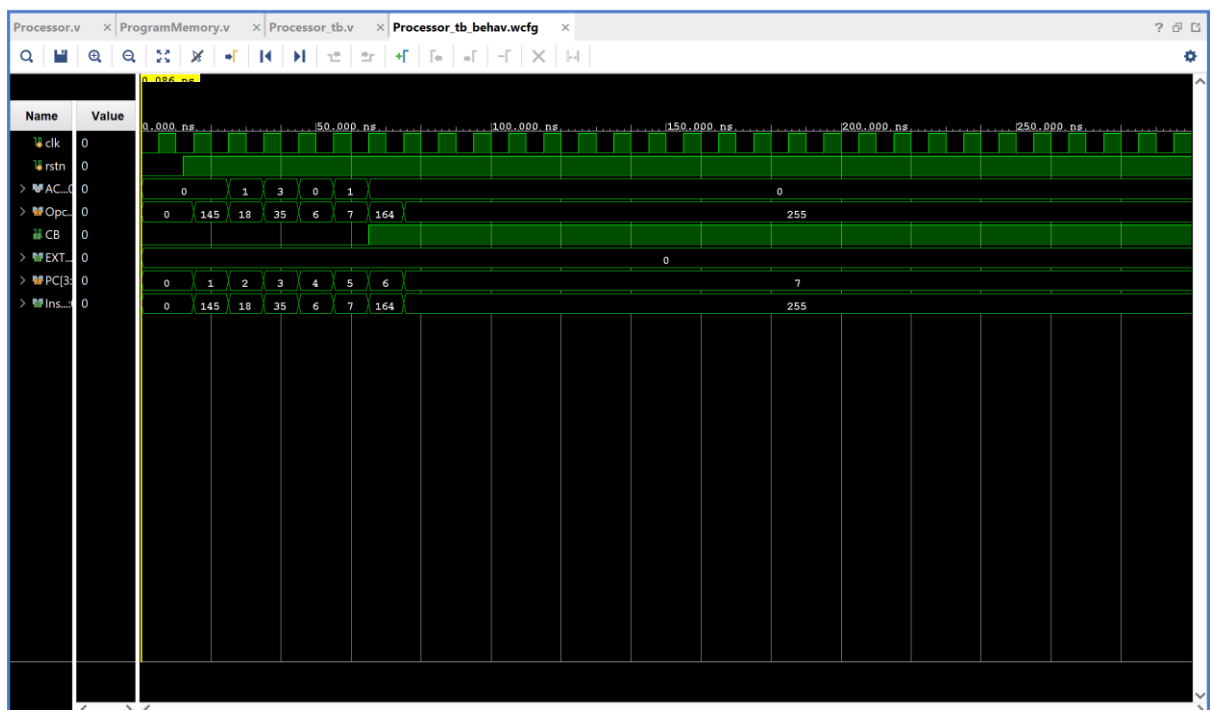


2. MUL, SUB, HLT

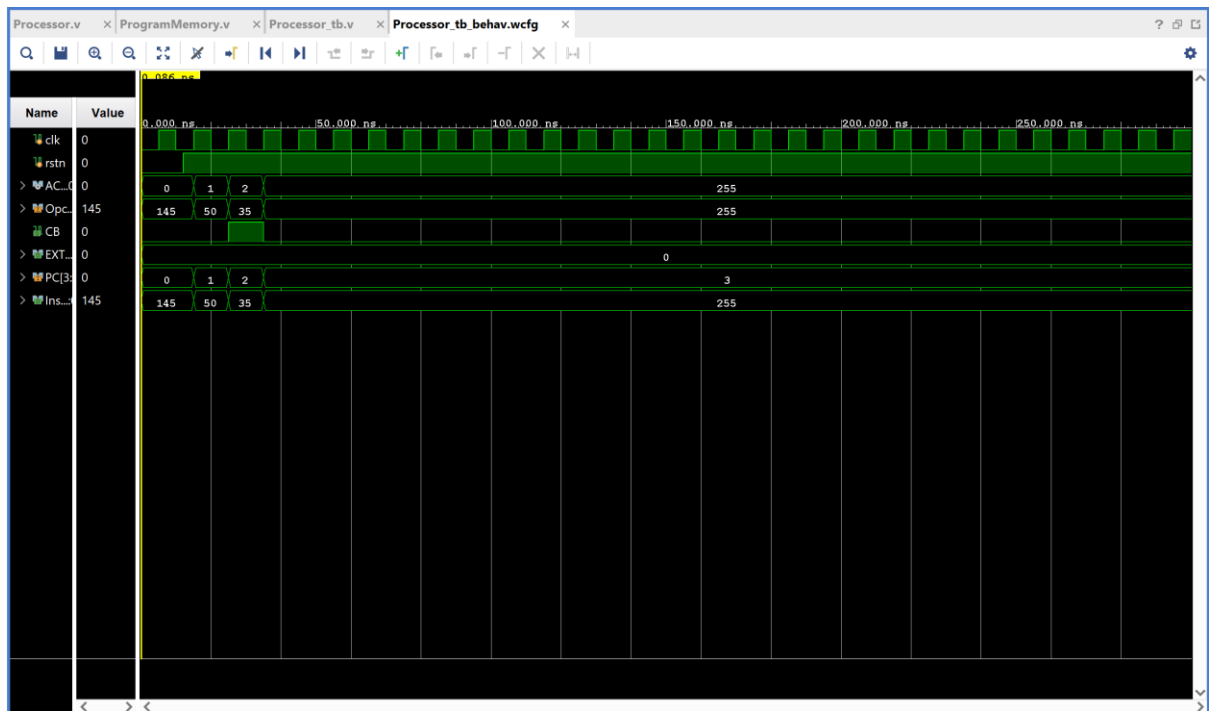


3. All shifts + AND, XRA, NOP, HLT

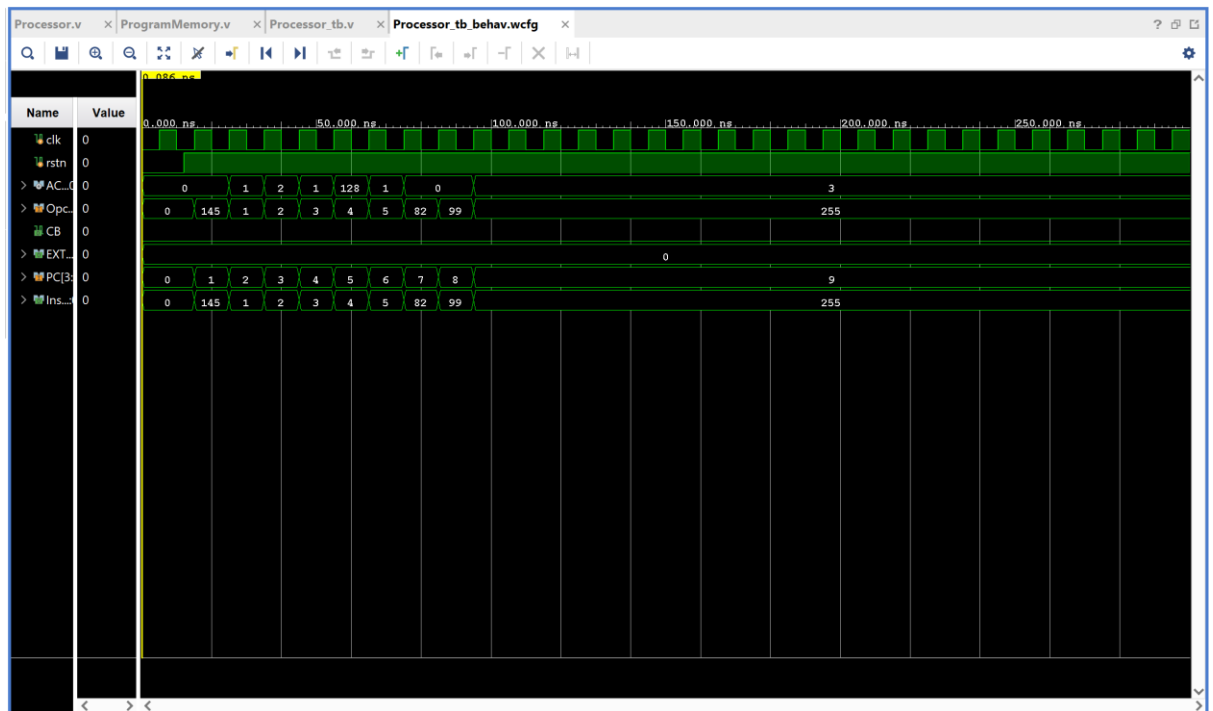


4. CMP, Br, Ret, MOV, HLT

 

5. Up Counter upto 15

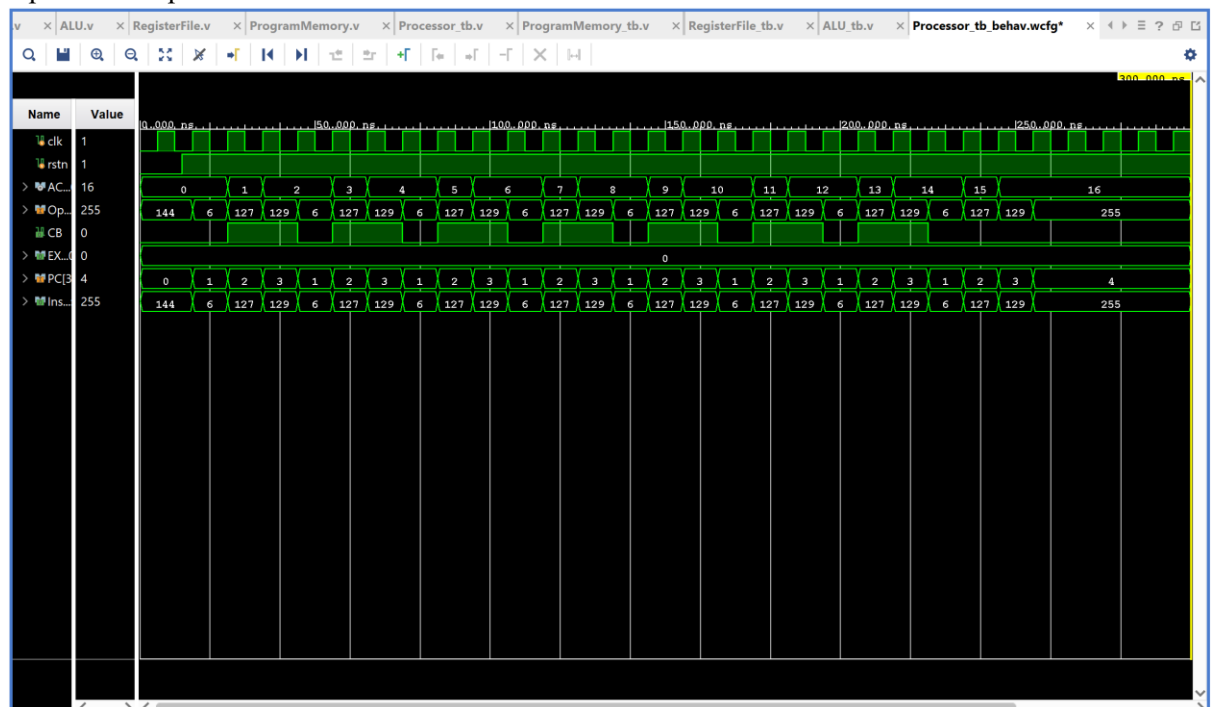

• Block Diagram

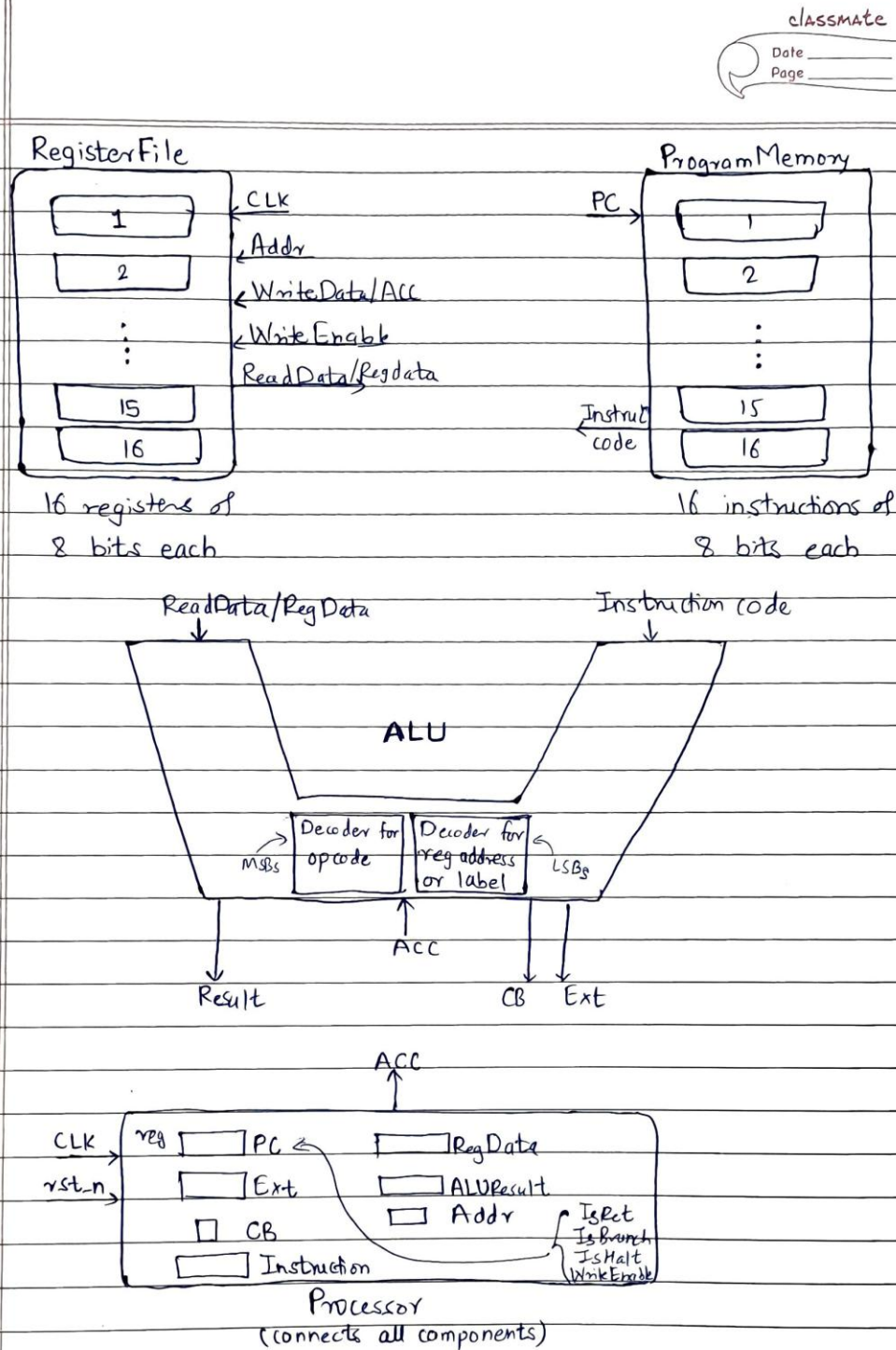

Block Diagram of Processor